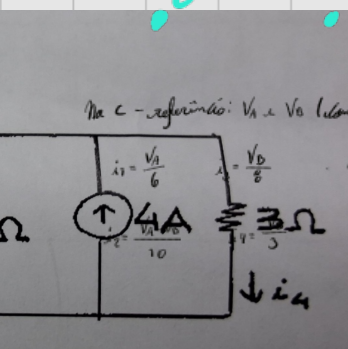


$$V_A - V_B$$

	Tensão	Corrente	Potência
$R_1 = 6\Omega$	27V	4,5A	123,5W
$R_2 = 10\Omega$	75V	7,5A	22,5W
$R_3 = 8\Omega$	72V	7,5A	18W
$R_4 = 3\Omega$	72V	4A	48W
fonte 6A	27V	6A	162W
fonte 4A	72V	4A	48W



Na C - referência: V_A e V_B (com relação a referência)

Na A: $i_1 + i_2 = 6$

$$\frac{V_A}{6} + \frac{V_A - V_B}{10} = 6$$

$$8V_A - 3V_B = 180$$

Na B: $i_2 + i_4 = i_3 + i_5$

$$\frac{V_A - V_B}{10} + 4 = \frac{V_B}{8} + \frac{V_A}{3}$$

$$-72V_A + 67V_B = 480$$

$$\begin{cases} 8V_A - 3V_B = 180 & \times 3 \rightarrow 24V_A - 9V_B = 540 \\ -72V_A + 67V_B = 480 & \times 3 \rightarrow -216V_A + 201V_B = 1440 \end{cases}$$

$$V_B = \frac{1500}{125} = 12 \rightarrow V_A = 27$$



- C como referência V_A e V_B $V = R \cdot i$ $i = \frac{V}{R}$

$$i_1 = \frac{V_A}{15} \quad i_2 = \frac{V_A}{60} \quad i_3 = \frac{V_A - V_B}{15} \quad i_4 = \frac{V_B}{3} \quad i_5 = \frac{V_B}{30}$$

* Na A:


$$i_1 + i_2 + i_3 = 8$$

$$9V_A - 4V_B = 480$$

* Na B:

$$i_4 + i_5 = i_3 + i_6$$

$$-2V_A + 13V_B = 75$$

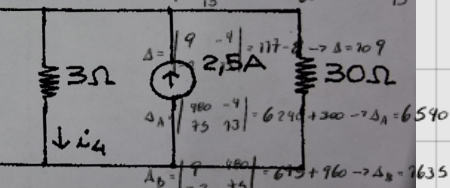

Tensão

$$R_1 = 75 \quad 60 \quad 4$$

$$R_2 = 60 \quad 60 \quad 1$$

$$R_3 = 75 \quad 45 \quad 3$$

$$R_4 = 3 \quad 75 \quad 5$$

$$R_5 = 30 \quad 75 \quad 0,5$$


$$\text{fonte } 8A \quad 60 \quad 8$$

$$\text{fonte } 2,5A \quad 75 \quad 2,5$$

	Tensão	Corrente	Potência
$R_1 = 75$	60	4	517,5W
$R_2 = 60$	60	1	
$R_3 = 75$	45	3	
$R_4 = 3$	75	5	
$R_5 = 30$	75	0,5	
fonte 8A	60	8	517,5W
fonte 2,5A	75	2,5	

$$V_A = \frac{\Delta A}{\Delta} = \frac{6540}{109} \rightarrow V_A = 60A$$
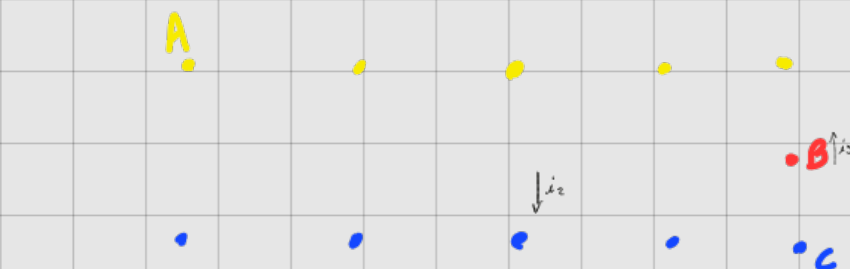
$$V_B = \frac{\Delta B}{\Delta} = \frac{7635}{109} \rightarrow V_B = 75V$$




* Na C como referência:


$$V_B = 40$$

* Na A: $10 + i_3 = i_1 + i_2 + i_4$
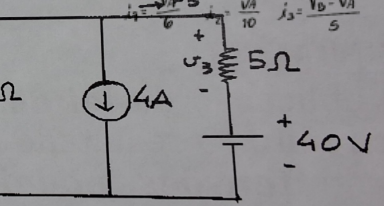
$$5V_A + 3V_A = 6V_B - 6V_A + 180 \rightarrow V_A = 30V$$



4)

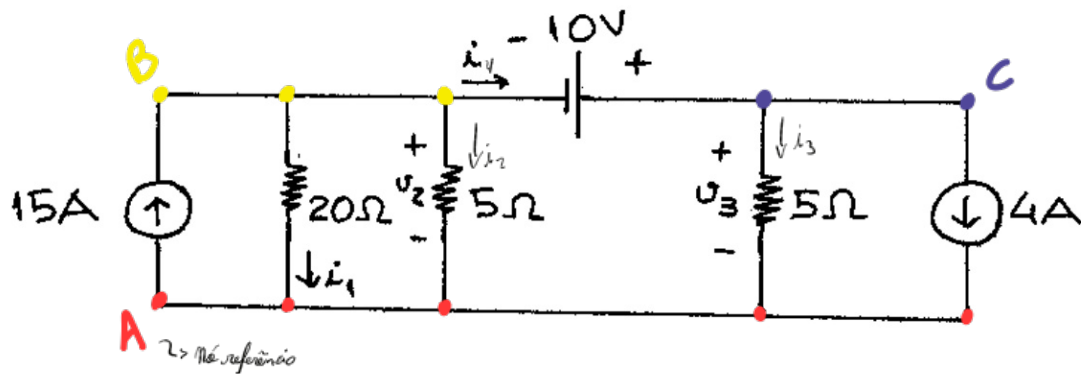

$$V = R \cdot i \rightarrow i = \frac{V}{R}$$

$$i_1 = \frac{V_B}{20} \quad i_2 = \frac{V_B}{5} \quad i_3 = \frac{V_C}{5}$$


* No. B: $i_1 + i_2 + i_3 = 15 \rightarrow i_1 + i_2 + i_3 + 4 = 19$

* No. C: $i_3 = i_3 + 4$

$$\frac{V_B}{20} + \frac{V_B}{5} + \frac{V_C}{5} = 11 \quad (I)$$

$$(I) \frac{V_B}{20} + \frac{V_B}{5} + \frac{V_C}{5} = 11 \xrightarrow{\times 20} V_B + 4V_B + 4(V_B + 20) = 220 \rightarrow 9V_B = 180 \rightarrow V_B = 20V \quad \therefore V_C = 30V$$

5)

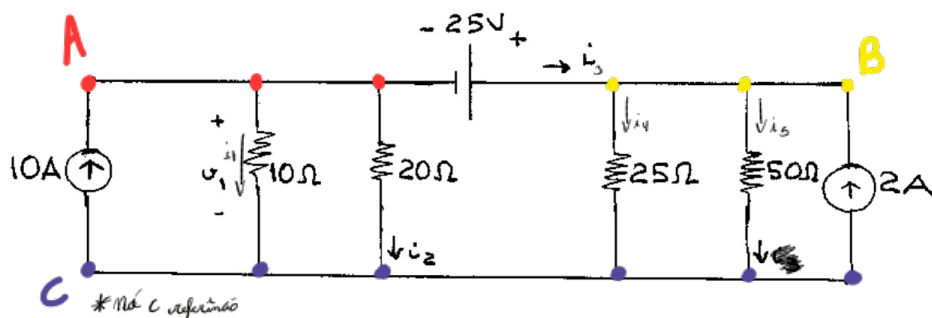

$$V = R \cdot i \rightarrow i = \frac{V}{R}$$

$$i_1 = \frac{V_A}{10} \quad i_2 = \frac{V_A}{20} \quad i_3 = \frac{V_B}{25} \quad i_4 = \frac{V_B}{50}$$

* No. A: $i_1 + i_2 + i_3 = 10 \rightarrow i_1 + i_2 + i_4 + i_5 = 12$

* No. B: $i_4 + i_5 = i_3 + 2$

$$\frac{V_A}{10} + \frac{V_A}{20} + \frac{V_B}{25} + \frac{V_B}{50} = 12$$


$$V_B - V_A = 25 \quad V_B = 25 + V_A$$

$$15V_A + 6V_B = 1200$$

$$15V_A + 6(V_A + 25) = 1200$$


$$21V_A = 1050 \rightarrow V_A = 50V \quad \therefore V_B = +5V$$

6)

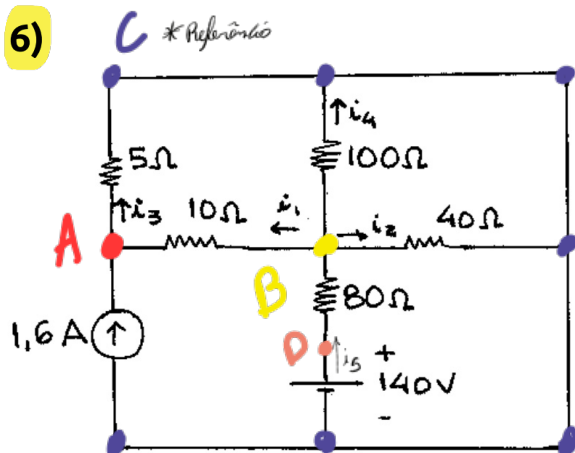

$$V = R \cdot i \rightarrow i = \frac{V}{R} \quad V_D = 190V$$

7) Circuito com fonte dependente:

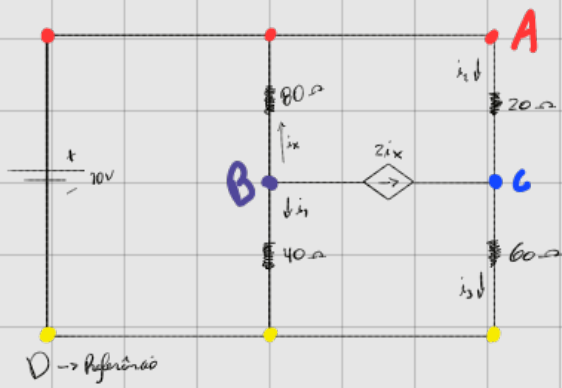

$$i_1 = \frac{V_B}{40} \quad i_2 = \frac{V_A - V_C}{20} \quad i_3 = \frac{V_C}{60} \quad i_4 = \frac{V_A - V_B}{80}$$

* Nó A: $V_A = 10V$

* Nó B:

$$i_4 + 2i_1 + i_2 = 0 \rightarrow \frac{3(V_A - V_B)}{80} + \frac{V_B}{40} = 0 \rightarrow V_B = 6V$$

* Nó C:

$$2i_1 + i_2 = i_3 \rightarrow \frac{2(V_B - V_A)}{80} + \frac{(V_A - V_C)}{20} = \frac{V_C}{60} \rightarrow 8V_C = 3V_B + 3V_A \rightarrow V_C = 6V$$



* Nó A: $V_A = 50V$

* Nó B:

$$i_1 + i_2 = i_3 + 3i_1 \rightarrow \frac{(V_B - V_C)}{2} + \frac{V_B}{8} = \frac{4 \cdot (V_A - V_B)}{6} \rightarrow 31V_B - 12V_C = 800$$

* Nó C:

$$3i_1 + i_3 = i_2 + 5 \rightarrow \frac{3 \cdot (V_A - V_B)}{6} + \frac{V_C}{4} = \frac{V_B - V_C}{2} + 5 \rightarrow 4V_B - 3V_C = 2V_A + 20 \rightarrow 4V_B - 3V_C = 80$$

$$\begin{cases} 31V_B - 12V_C = 800 \\ 4V_B - 3V_C = 80 \end{cases} \rightarrow \begin{matrix} V_B = 32V \\ V_C = 16V \end{matrix} \quad \text{e} \quad V_A = 50V$$